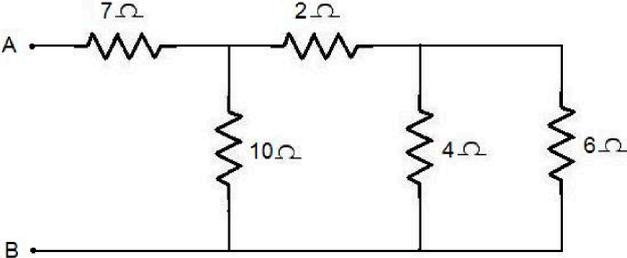
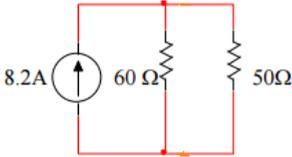
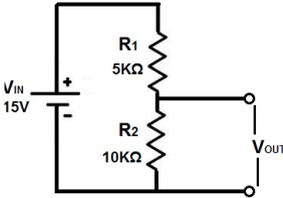
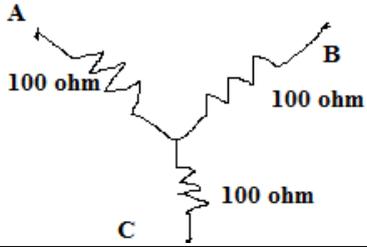


VELAMMAL COLLEGE OF ENGINEERING AND TECHNOLOGY, MADURAI – 625 009			
Department of Electronics and Communication Engineering			
<i>INTERNAL ASSESSMENT - I</i>			
Branch	ECE	Year/Sem./Sec.	I/II/A,B& C
Course Code	21ECE102	Date	
Course Name	Circuit Analysis	Max. marks	50
Course Incharge	Dr. K. Kavitha , Dr. S. Gandhimathi @ Usha & Ms. J. Rajeswari	Time	01:40 Hours






PART A




Sl.No	QUESTION	K	CO	Marks
1	Define Ohm's Law and its limitations.	K1	CO1	2
1	Define Kirchoff's Voltage law.	K1	CO1	2
1	Define Kirchoff's Current law.	K1	CO1	2
2	The resistance of two wires is 25Ω when connected in series and 6Ω when connected in parallel. Find the resistance of each wire.	K1	CO1	2
2	Solve the equivalent resistance between A and B in the given circuit 	K3	CO1	2
2	Explain current division rule.	K2	CO1	2
3	Show the expression of equivalent resistance for 'n'- number of resistors in parallel connection	K1	CO1	2
3	Compute the current in 50Ω resistor in the given circuit 	K2	CO1	2
3	Define voltage division rule	K1	CO1	2
4	Two 20Ω resistors are connected in series. When a resistor R is connected across one of them, the total resistance of the network becomes 30Ω . Find the value of R.	K1	CO1	2
4	Compute the voltage V_{out} . 	K2	CO1	2
4	Compare mesh and nodal analysis.	K2	CO1	2
5	What are the types of sources?	K1	CO1	2
5	Compute the equivalent resistance for the circuit shown:	K2	CO1	2




5	<p>Transform the following voltage source to current source:</p>	K2	CO1	2
6	<p>Find the voltage source equivalent for the circuit:</p>	K1	CO1	2
6	<p>Compute the current through R3 in the circuit:</p>	K2	CO1	2
6	The equivalent resistance of three resistors in series is 750 ohms. Two of the resistors are 40 and 410 ohms. What must be the ohmic resistance of the third resistor?	K1	CO1	2
7	Define Superposition theorem.	K1	CO2	2
7	What is the limitation of superposition theorem?	K1	CO2	2
7	Given that the resistors Ra, Rb and Rc are connected electrically in star. Write the equations for resistors in equivalent delta.	K1	CO2	2
8	A Y-connected resistive network consists of 3 ohm in each arm. Translate to the equivalent delta-connected network and insert the values.	K2	CO2	2
8	Translate to equivalent delta circuit for the given star network.	K2	CO2	2

				
8	Each of the three arms of a delta connected network has resistance of 4ohm. Translate to equivalent star connected network.	K2	CO2	2

PART B

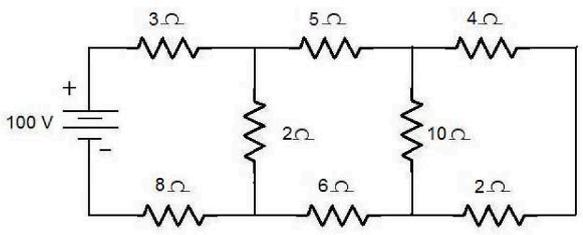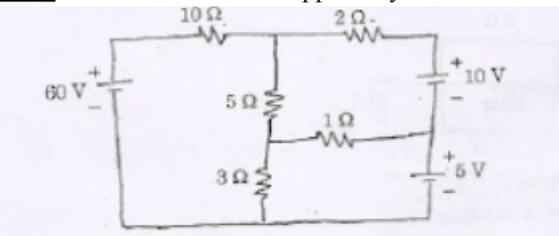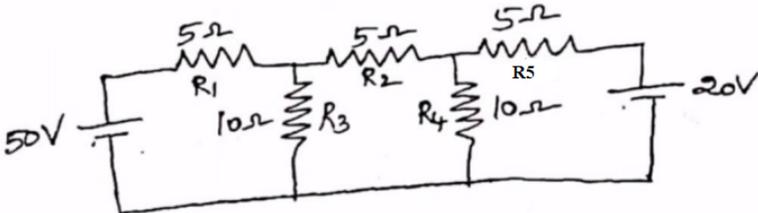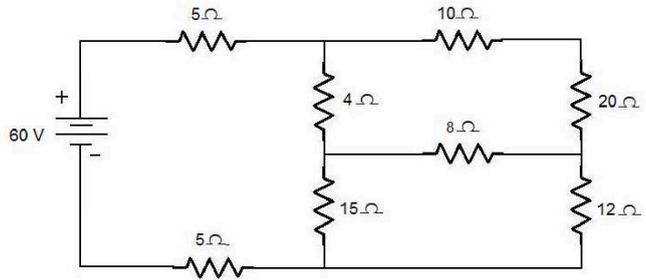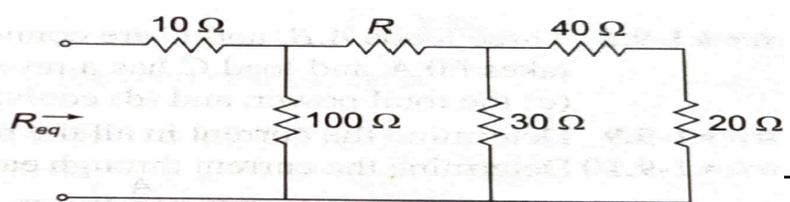Sl.No	QUESTION	K	CO	Marks
9	<p>Solve and find the current through each branch using mesh analysis</p> 	K3	CO1	13
9	<p>Solve and find the current supplied by the source using mesh analysis</p> 	K3	CO1	13
9	<p>Use nodal voltage method to find the current in the resistances R3 and R4 in the network shown below.</p> 	K3	CO1	13
9	<p>In the network shown below, solve and find the current delivered by the battery.</p> 	K3	CO1	13
10	<p>In the network shown in below fig (a) let $R=80\Omega$, find R_{eq} (b) find R if $R_{eq}=80\Omega$ (c) find R if $R=R_{eq}$</p> 	K3	CO1	13

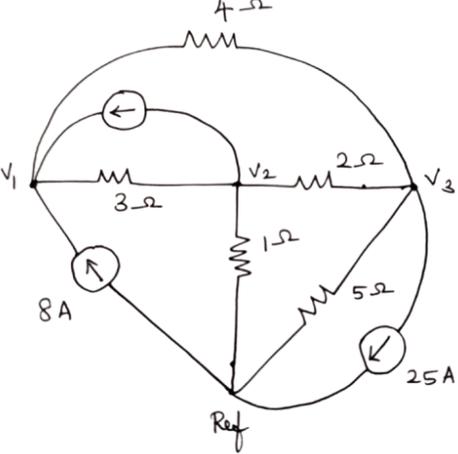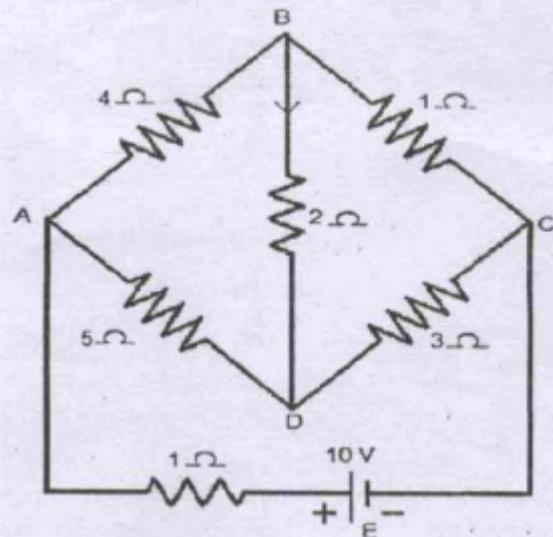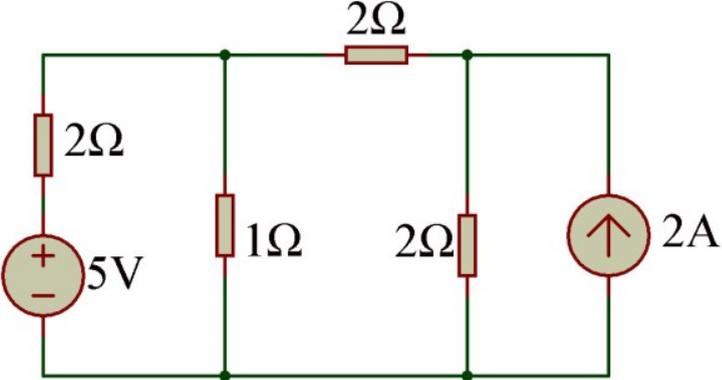10	<p>Solve and Find the node voltages in the circuit</p> 	K3	CO1	13
10	<p>Identify the current through 2 ohm resistor and the total current delivered by the battery.</p> 	K3	CO1	13
10	<p>Solve and Find the current in 1 ohms resistor</p> 	K3	CO1	13

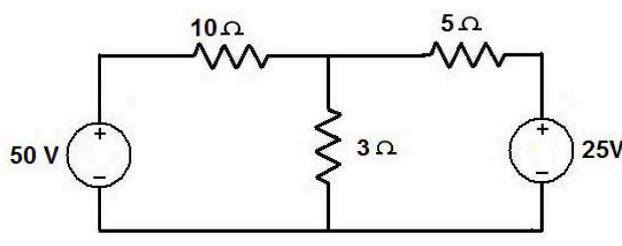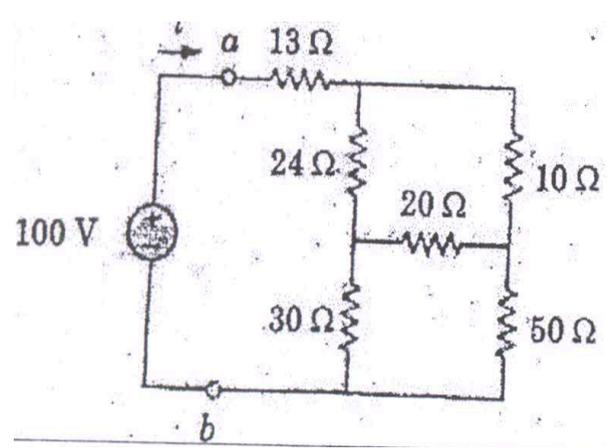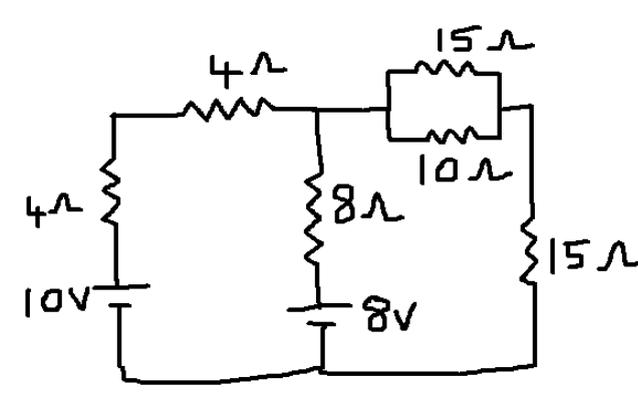Sl.No	QUESTION	K	CO	Marks
11	<p>Solve and find the current in each resistor using superposition principle of the circuit</p> 	K3	CO2	8
11	<p>Make use of star to delta transformation to determine the equivalent resistance between terminals ab for the given circuit</p> 	K3	CO2	8
11	<p>Identify the current in 10 ohms resistor using superposition theorem</p> 	K3	CO2	8
11	<p>Make use of star-delta transformation to determine the equivalent resistance of the circuit shown in below fig</p>	K3	CO2	8

